

APJ Abdul Kalam Technological University

Ernakulam II Cluster

First Semester M.Tech Degree Examination December 2017

05EC 6005 ADVANCED DIGITAL DESIGN

Time: 3 hrs.

Max. Marks: 60

- 1) a) Draw a state diagram for an FSM that has an input X and an output Y. Whenever X changes from 0 to 1, Y should become 1 for two clock cycles and then return to 0 even if X is still 1. (4 Marks)
- b) What are ASM Charts? Realize the following ASM in figure 1 using D Flip-Flops.

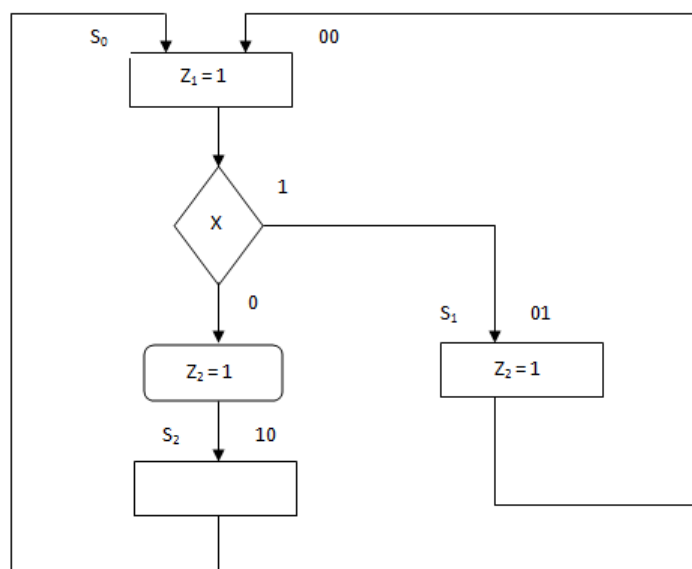


Figure 1

(8 Marks)

- 2) a) Use magnitude comparators and logic to design a circuit that outputs 1 when an 8-bit input 'a' is in between 75 and 100(both numbers inclusive). (6 Marks)
- b) Design an ALU with two 8 bit inputs A and B, and control signals x, y and z. The ALU should support the operations in the table below. Use an 8-bit adder and an arithmetic logic extender

Inputs			Operation
x	y	z	
0	0	0	$S = A - B$
0	0	1	$S = A + B$
0	1	0	$S = A * 8$
0	1	1	$S = A / 8$
1	0	0	$S = A \text{ NAND } B$ (bitwise NAND)
1	0	1	$S = A \text{ XOR } B$ (bitwise XOR)
1	1	0	$S = \text{Reverse } A$ (bit reversal)
1	1	1	$S = \text{NOT } A$ (bitwise complement)

(6 Marks)

- 3) a) Design a laser- based distance measurement system, where a laser is pointed at the object of interest. The laser 's' briefly turned on and a timer is started. The laser light, travelling at the speed of light, travels to the object and reflects back. A sensor detects the reflection of the laser light, causing the timer to stop. Knowing the time T taken by the light to travel to the object and back, distance can be calculated. Use RTL design process. (12 Marks)
- b) Compose a 16x1 MUX from 2x1 MUXs. (6 Marks)

OR

- 4) a) Determine the register-to-register critical path and the longest path delay for the circuit given in figure 2. Assume no wire delay, and the following component delays: Multipliers take 5 ns, Adders take 2 ns, Multiplexers take 1ns. Based on the longest path delay obtained, what should the frequency of this circuit be? (6 Marks)

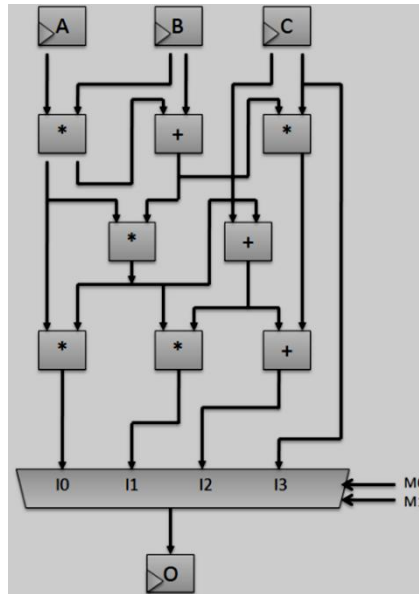


Figure 2

- b) Compose a 4x16 decoder with enable from 2x4 decoders with enable. (6 Marks)
- c) Summarize the main differences between DRAM and SRAM memories. (6 Marks)
- 5) a) Compare Moore and Mealey FSM. Design an FSM using mealey and moore model for a wrist watch that can perform the following operations a) display present time, b) set alarm c)display date d)act as a stop watch.The FSM should sequence to the next register, in the order listed above, each time a button b is pressed (assume b is synchronized with the clock as to be high for only 1 clock cycle on each unique button press). The FSM should set an output p to 1 each time the button is pressed, causing an audible beep to sound. (12 Marks)
- b) Reduce the number of states for the FSM given in figure 3.

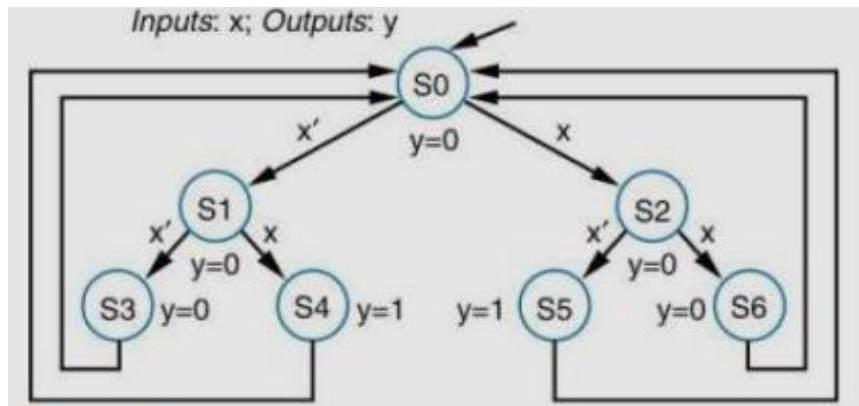


Figure 3

(6 Marks)

OR

- 6) a) Define state encoding. Discuss the various methods of state encoding. (8 Marks)
- b) Design a circuit that repeatedly generates the output sequence 0,1,1,1. Encode the states using minimal binary encoding and one hot encoding and compare the size and delay.

(10 Marks)
