

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
FIFTH SEMESTER B.TECH DEGREE EXAMINATION, APRIL 2018

Course Code: EC307

Course Name: POWER ELECTRONICS & INSTRUMENTATION (EC)

Max. Marks: 100

Duration: 3 Hours

PART A

Answer any two full questions, each carries 15 marks

- | | | Marks |
|---|---|-------|
| 1 | a) Explain the constructional details and the working of power MOSFET. Also bring out the difference between low power MOSFET and power MOSFET. | (10) |
| | b) Explain the principle of operation of boost converter. | (5) |
| 2 | a) Define softness factor of power diodes. | (2) |
| | b) Describe the working of IGBT. How does Latch-up occur in IGBT? | (5) |
| | c) Explain the switching waveform of power transistor. Also describe its input and output characteristics. | (8) |
| 3 | a) Explain the working principle of buck converter and illustrate the operation with the inductor current and the switching waveforms. | (8) |
| | b) Explain the principle of operation of full bridge isolated converter topology. | (7) |

PART B

Answer any two full questions, each carries 15 marks

- | | | |
|---|---|------|
| 4 | a) Explain the working principle of push pull inverter. | (5) |
| | b) Describe the principle of operation of Wheatstone bridge and derive the expression for unknown resistance. | (8) |
| | c) Distinguish between choppers and inverters. | (2) |
| 5 | a) Explain the space vector modulation in three phase inverters. | (10) |
| | b) Explain Self oscillating type and driven type inverters. | (5) |
| 6 | a) Explain different classification of instruments. | (12) |
| | b) What is the criterion for balance of Schering's bridge? | (3) |

PART C

Answer any two full questions, each carries 20 marks

- | | | |
|---|---|------|
| 7 | a) Explain the range changing circuit of digital voltmeter. | (5) |
| | b) Explain the principle of operation of resistance transducer. Explain the difference between bonded and unbounded type strain gauges. | (10) |
| | c) Explain the block diagram of swept super heterodyne spectrum analyser. | (5) |
| 8 | a) Explain the principle of operation of LVDT. List out its advantages. | (7) |
| | b) What are the major guidelines for the selection of transducers? | (5) |
| | c) Explain about any two types of capacitive transducers. | (8) |
| 9 | a) Explain the block diagram of frequency synthesizer with waveforms. | (6) |
| | b) Draw and explain the basic block diagram of DSO. Sketch the system waveforms and list out its applications. | (10) |
| | c) Explain about ramp type digital voltmeter. | (4) |
