

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

B.Tech S4 (S) Exam Sept 2020

Course Code: EE204**Course Name: DIGITAL ELECTRONICS AND LOGIC DESIGN (EE)**

Max. Marks: 100

Duration: 3 Hours

PART A*Answer all questions, each carries 5 marks*

Marks

- | | | |
|---|---|-----|
| 1 | Convert | |
| | a) $(2469)_{10}$ in to BCD. | (1) |
| | b) $(735)_8$ to decimal. | (1) |
| | c) $(650)_{10}$ to hexadecimal, gray and binary. | (3) |
| 2 | Using Boolean algebra prove that $(A + B)(A' + C) = AC + A'B$. | (5) |
| 3 | Design a full subtractor logic circuit. | (5) |
| 4 | Explain SISO and SIPO shift registers. | (5) |
| 5 | Draw the logic diagram and timing sequence of a 4-bit ring counter. | (5) |
| 6 | Prepare the state table and derive the logic expression for each flip flop input for a 3-bit binary synchronous down counter using T flip flop? | (5) |
| 7 | Explain the working of R-2R ladder type DAC. | (5) |
| 8 | Compare PAL and PLA. | (5) |

PART B*Answer any two questions, each carries 10 marks*

- | | | |
|----|--|-----|
| 9 | a) Given $X = 38_{10}$ and $Y = 105_{10}$. Using 2's complement method calculate (i) $X - Y$ (ii) $Y - X$ | (5) |
| | b) How is the error detection and correction carried out using parity method in digital data transmission? | (5) |
| 10 | a) Using K map, minimize the expression
$F(A,B,C,D) = \sum m(1,2,3,8,14,15) + d(0,4,6,10)$. | (5) |
| | b) Realize the Boolean expression $Z = ABC + AD + CD'$ using NAND gates only. | (5) |
| 11 | a) Explain a CMOS NAND gate . | (5) |
| | b) Find the standard Product of Sum (POS) for the logic expression
$F = (A + B'C)C$ | (5) |

PART C

Answer any two questions, each carries 10 marks

- 12 Develop a 3-stage carry look ahead adder and implement using basic gates. (10)
- 13 Realize the following function $F(A,B,C,D) = \sum m(1,3,4,10,11,12,13)$ using
(i) 4 X 1 MUX (ii) 8 X 1 MUX (10)
- 14 a) Explain a 3 bit asynchronous up counter. Draw the timing diagram and truth table. (5)
- b) Draw the logic diagram of J-K flip flop and explain it. What is the advantage of J-K flip flop over S-R flip flop. (5)

PART D

Answer any two questions, each carries 10 marks

- 15 Design a 3-bit gray code synchronous counter using J-K flip flop and explain the steps in detail. (10)
- 16 a) Compare Mealy and Moore state machine models with example. (5)
- b) Differentiate between ROM and RAM. (5)
- 17 a) Implement a full adder circuit using VHDL (5)
- b) Explain the working of successive approximation ADC. Mention the advantages and disadvantages. (5)
