

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
Third Semester B.Tech Degree (S,FE) Examination December 2020

**Course Code: EE201**

**Course Name: CIRCUITS AND NETWORKS**

Max. Marks: 100

Duration: 3 Hours

**PART A**

*Answer all questions, each carries 5 marks.*


Marks

- |   |  |     |
|---|--|-----|
| 1 | State and explain maximum power transfer theorem as applicable to AC networks with load $Z_L = R_L + jX_L$ . | (5) |
| 2 | List any three properties of incidence matrix associated with graph theory.                                  | (5) |
| 3 | Define time constant and explain its significance.   | (5) |
| 4 | Explain the terms magnetic coupling and dot convention.  | (5) |
| 5 | Explain open circuit parameters of a 2 port network.   | (5) |
| 6 | State the conditions a 2 port network to be reciprocal with respect to z, y, h, ABCD parameters.             | (5) |
| 7 | State the conditions for a polynomial to be Hurwitz .  | (5) |
| 8 | Write any five properties of impedance function of RL network.   | (5) |

**PART B**

*Answer any two full questions, each carries 10 marks.*

- |   |   |      |
|---|---|------|
| 9 | Determine the load current $I_L$ by using Norton's theorem. | (10) |
|---|---|------|

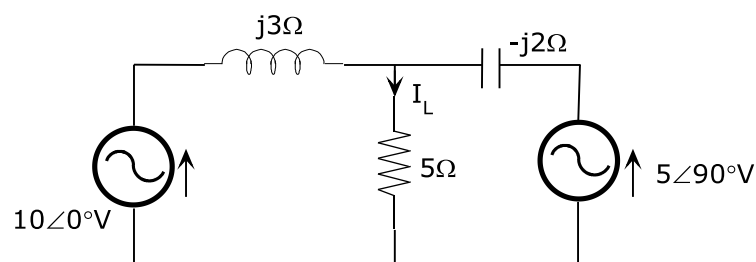


- |    |  |     |
|----|--|-----|
| 10 | a) State and explain superposition theorem.  | (5) |
|    | b) A reduced incidence matrix of a graph is given by<br>Obtain number of possible trees. | (5) |

$$[A] = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ -1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix}$$

- |    |  |      |
|----|--|------|
| 11 | For the graph shown below, select a tree with [1, 2, 3, 4] as twigs and [5, 6, 7] as | (10) |
|----|--|------|

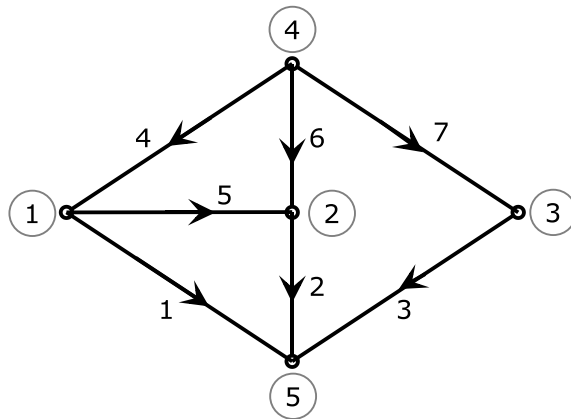
links. Obtain fundamental tie-set and cut-set matrices for the graph.



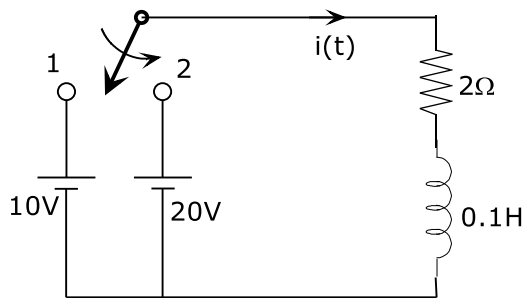**PART C**

*Answer any two full questions, each carries 10 marks.*

- 12 Determine the current  $i(t)$  when the switch is moved from position 1 to position 2 at  $t=0$ . The switch has been in position 1 for a long time to get steady state values. (10)




- 13 Derive expression for transient current in a RL series circuit excited with i) DC voltage and ii) AC sinusoidal voltage by applying Laplace transform. (10)
- 14 a) Two inductively coupled coils have self inductances  $L_1 = 50 \text{ mH}$  and  $L_2 = 200 \text{ mH}$ . (5)
- i) Find the value of mutual inductance between coils if the coefficient of coupling is 0.5.
  - ii) What is the maximum possible mutual inductance?
- b) Plot the transient response of RLC series circuit for various damping conditions with DC excitation. (5)

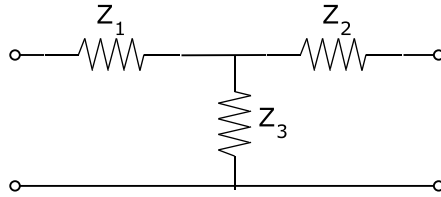**PART D**


*Answer any twofull questions, each carries 10 marks.*

- 15 a) Find Z parameters of the given two port network. The impedances are  $Z_1=5\text{k}\Omega$ ,  $Z_2=3\text{k}\Omega$ ,  $Z_3=12\text{k}\Omega$ . (6)



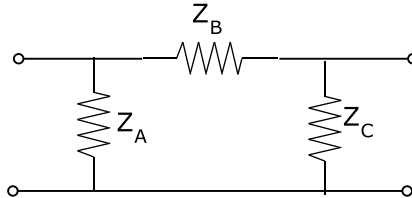b) Given  $Z_{11} = 6\Omega$ ,  $Z_{22} = 4\Omega$ ,  $Z_{12} = Z_{21} = 3\Omega$ . Compute ABCD parameters. (4)

16 a) Determine hybrid parameters. Given ,  $Z_A = Z_B = Z_C = 1k\Omega$  (5)



b) Check whether the polynomial  $P(S) = s^4 + s^3 + 2s^2 + 4s + 1$  is Hurwitz. (5)

17 Driving point impedance is given by  $Z(s) = \frac{s(s^2+4)(s^2+6)}{(s^2+1)(s^2+5)}$  (10)

Obtain first form of Cauer Network.

\*\*\*\*\*