

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Fifth Semester B.Tech Degree Regular and Supplementary Examination December 2020

Course Code: EC361**Course Name: DIGITAL SYSTEM DESIGN**


Max. Marks: 100

Duration: 3 Hours

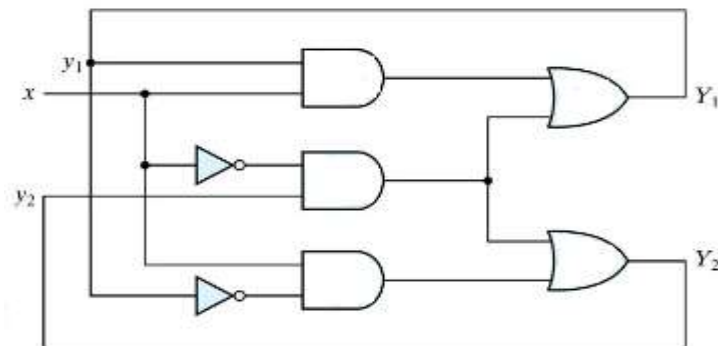PART A*Answer any two full questions, each carries 15 marks.*

Marks


- 1 a) What are iterative circuits? Design an iterative circuit for a 4-bit ripple carry adder. (7)
- b) Design a CSSN using JK-FF having a single input line 'x' in which binary symbols 1 and 0 are applied. The network is to produce an output '1' with each 3rd multiple of 0 detected. All other times the output has to remain at '0'. Write the proper sample sequence before starting the design. (8)
- 2 a) Analyse the following fundamental mode asynchronous sequential circuit



(7)

- b) Design a coffee vending machine. The machine is to accept 5 and 10 rupees notes only. The amount for a coffee is 15 rupees. (It is not necessary that the machine gives the balance amount). (8)
- 3 a) Design a fundamental mode asynchronous sequential circuit meeting the following requirements:
- there are two inputs x and y, and single output z. (8)
 - x and y never change simultaneously.
 - the output is to be same as x if y = 1. However, if y = 0, the output should remain fixed at its last value before y became 0.

b) Analyse the below given CSSN.

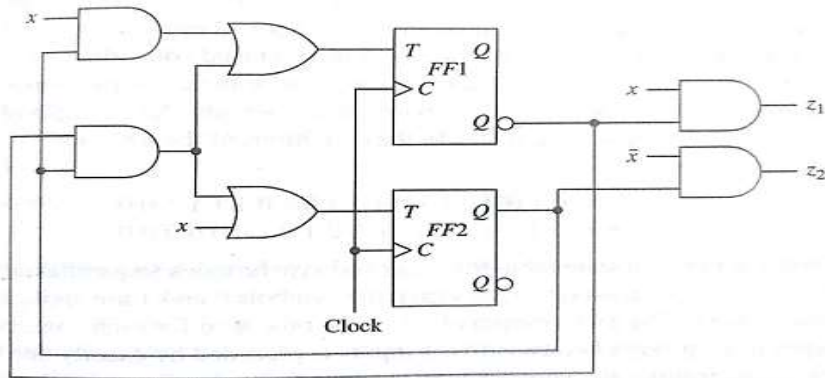


(7)

PART B


Answer any two full questions, each carries 15 marks.

4 a) What do you mean by clock skew? Explain setup time, hold time, setup and hold violations with a neat timing diagram. How can we use clock skew to avoid the setup and hold violations? Justify. (8)

 b) Differentiate between static and dynamic hazards. What hazard exists in the circuit given below. Also derive the hazard free circuit. (7)




 5 a) Find the minimal complete test for x0, x1, x2 and x3, x4 and x5 for the below given circuit using the Fault table method. (8)



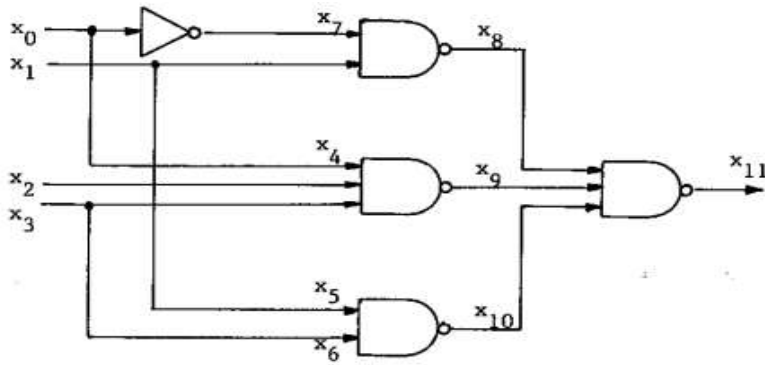b) What is a fault? How are faults classified? Define the terms: fault detection, fault location, test vector, Essential test vector, selective test vector and minimal complete test set. Explain the steps involved in the testing process. (7)

6 a) Using Path sensitisation method, find the test vectors for detecting SA0 and SA1 faults at x7 and x9. (8)



- b) Explain essential hazards in asynchronous sequential networks with example. (7)
 What are the constraints to be satisfied to avoid essential hazards?

PART C

Answer any two full questions, each carries 20 marks.

- 7 a) Explain different kinds of PLA folding. (10)
 b) Describe the different test generation techniques for PLA. (10)
- 8 a) Examine the Input/output block of typical FPGA with the aid of a diagram. (10)
 b) Describe the architecture of XC9500 CPLD with the help of a block diagram. (10)
- 9 a) Draw the simplified block diagram of Xilinx XC4000 configurable logic block (10)
 and explain the various sections.
 b) Write short notes on following: (10)
 i) Design for testability ii) Built in self-test iii) PLA folding algorithm
