

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Seventh Semester B.Tech Degree Examination (Regular and Supplementary), December 2020

Course Code: EC461**Course Name: MICROWAVE DEVICES AND CIRCUITS**

Max. Marks: 100

Duration: 3 Hours

PART A*Answer any two full questions, each carries 15 marks.*

Marks

- | | | | |
|---|----|---|------|
| 1 | a) | With neat diagram explain Two-Valley model theory of Gunn Diode. | (10) |
| | b) | What are the Characteristics and advantages of microwaves? | (5) |
| 2 | a) | Discuss in detail the term stability with respect to microwave amplifier. | (10) |
| | b) | Explain the biasing of microwave bipolar transistor. | (5) |
| 3 | a) | Classify the modes of operation of Microwave Bipolar transistor. | (8) |
| | b) | Derive an expression for power output and efficiency of IMPATT diode. | (7) |

PART B*Answer any two full questions, each carries 15 marks.*

- | | | | |
|---|----|---|------|
| 4 | a) | Explain the concept of signal flow graph of a two port network. What are the rules to decompose a signal flow graph? | (8) |
| | b) | Write a short note on Impedance and Admittance Matrices. | (7) |
| 5 | a) | A five element maximally flat Butterworth low pass filter is to be designed for use in 50Ω circuit. Its 3 dB point is 500 MHz. Calculate its component value. | (10) |
| | b) | What are terminated periodic structure? Explain. | (5) |
| 6 | a) | With neat diagrams and relevant equations, explain about the theory of small reflections. | (8) |
| | b) | Explain Richard's Transformation and Kuroda's identities. | (7) |

PART C*Answer any two full questions, each carries 20 marks.*

- | | | | |
|---|----|---|-----|
| 7 | a) | Explain about the materials used in Monolithic MIC. | (8) |
|---|----|---|-----|

- b) Differentiate strip line and microstrip line. (6)
- c) Discuss in detail about the various losses in microstrip lines. (6)
- 8 a) Explain attenuators with neat diagram. (10)
- b) Discuss briefly about capacitors. (5)
- c) Explain switched line phase shifters with neat diagrams. (5)
- 9 a) Compare Monolithic MICs with Hybrid MICs. (10)
- b) With neat diagram explain SPDT Transmit – Receive switch. (6)
- c) Explain the configuration of ferrite circulators. (4)
