

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
Second Semester B.Tech Degree Examination June 2022 (2019 scheme)

**Course Code: EST130**

**Course Name: BASICS OF ELECTRICAL AND ELECTRONICS ENGINEERING**  
(2019 -Scheme)

**PART I : BASIC ELECTRICAL ENGINEERING**

Max. Marks: 50

Duration: 90 min

**PART A**

*Answer all questions, each carries 4 marks*

Marks


- |   |   |     |
|---|---|-----|
| 1 | Three resistors, $6\Omega$ , $10\Omega$ and $15\Omega$ are connected in star configuration. Obtain the equivalent resistance in a delta configuration.  | (4) |
| 2 | Two coils A and B of 500 and 750 turns respectively are connected in series on the same magnetic circuit of reluctance $1.55 \times 10^6$ AT/Wb. Assuming that there is no flux leakage, calculate (i) self-inductance of each coil and (ii) mutual inductance between coils. | (4) |
| 3 | Explain the concept of statically induced emf in a magnetic circuit.  | (4) |
| 4 | Derive the relation between line and phase voltages in a 3 phase star connected system.   | (4) |
| 5 | Define the following terms with an example:<br>a) Phase b) Phase difference   | (4) |

**PART B**

*Answer one full question from each module, each question carries 10 marks.*

**MODULE 1**

- 6 Find the mesh currents  $i_1$ ,  $i_2$ ,  $i_3$  in the circuit shown in Figure 1 by performing mesh analysis (10)

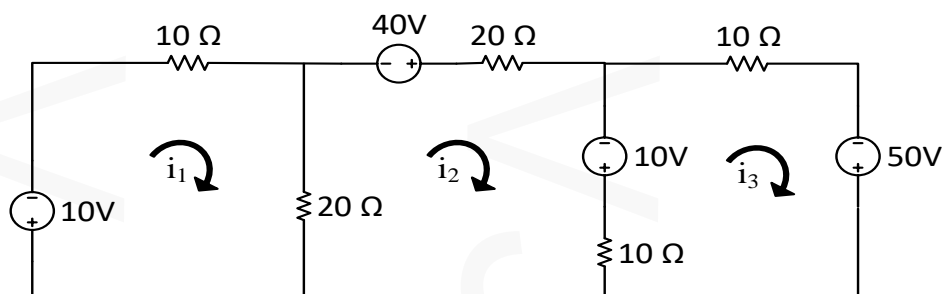

**Figure 1**

OR

- 7 Find the node voltages  $v_1$  and  $v_2$  in the circuit given in Fig. 2. Also find the power dissipated in the  $4\Omega$  resistor. (10)

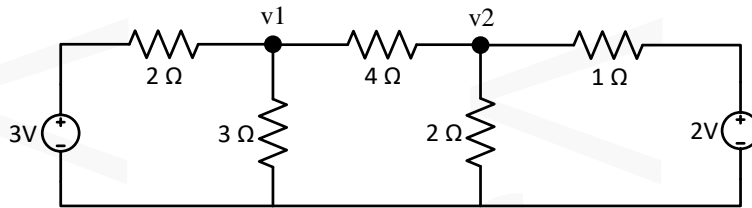


Figure 2

## MODULE 2

- 8 a A core forms a closed magnetic loop of path length 32 cm. Half of this path has a cross-sectional area of  $2\text{ cm}^2$  and relative permeability 800. The other half has a cross-sectional area of  $4\text{ cm}^2$  and relative permeability 400. Find the current needed to produce a flux of  $0.4\text{ Wb}$  in the core if it is wound with 1000 turns of insulated wire. Ignore leakage and fringing effects. (6)
- b Compare electric and magnetic circuits. (4)

OR

- 9 a An iron ring of cross-sectional area  $6\text{ cm}^2$  is wound with a wire of 100 turns and has a saw cut of 2 mm. Calculate the magnetising current required to produce a flux of  $0.1\text{ mWb}$ . if mean length of magnetic path is 30 cm and relative permeability of iron is 470. (8)
- b Define the terms relative permeability and flux density and give the relation between the two terms. (2)

## MODULE 3

- 10 Explain with phasor diagram instantaneous power when alternating current is supplied through a series R-L circuit. Also draw the impedance triangle and write an expression for active, reactive and apparent power in R-L circuit. (10)

OR

- 11 A balanced three phase load has per phase impedance of  $(30 + j50)\text{ ohm}$ . if the load is connected across 400 V, 3 phase supply, find (i) Phase current (ii) line current (iii) power supplied to the load when it is connected in (a) star (b) delta. (10)

\*\*\*\*

**PART 2 : BASIC ELECTRONICS ENGINEERING**

Max. Marks: 50

Duration: 90 min

**PART A**

*Answer all questions, each carries 4 marks*

Marks

- 12 Draw the symbol of resistor and explain any three specifications. (4)
- 13 For an NPN Transistor,  $\alpha = 0.98$ ,  $I_B = 100 \mu A$ , Find  $I_E$  and  $I_C$ . (4)
- 14 Explain the action of shunt capacitor filter. (4)
- 15 Explain the working principle of Zener voltage regulator. (4)
- 16 Differentiate between amplitude modulation (AM) and frequency modulation (FM). (4)

**PART B**

*Answer one full question from each module, each question carries 10 marks.*

**MODULE 4**

- 17 a Explain with necessary diagrams, the principle of operation of NPN transistor (5)
- b Describe the colour coding of a resistor with example. (5)

**OR**

- 18 a Draw the circuit diagram of a common emitter amplifier. (3)
- b Explain the input and output characteristics of common emitter configuration with neat diagrams (7)

**MODULE 5**

- 19 Describe the components of a DC power supply using a neat block diagram. (10)

**OR**

- 20 Explain the working of RC coupled amplifier with circuit diagram and relevant waveforms. Also explain the frequency response of RC coupled amplifier. (10)

**MODULE 6**

- 21 a Explain the concept of cells in cellular communication. (3)
- b Draw the block diagram of GSM and explain the principle of operation. (7)

**OR**

- 22 a Describe the principle and working of an antenna. (6)
- b What is frequency reuse? Explain with a diagram. (4)

\*\*\*\*